


## **NMOS Schematic**

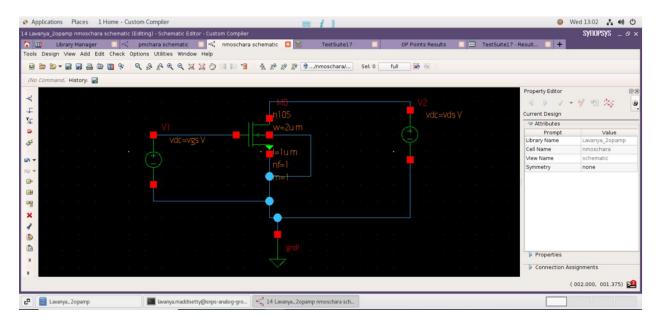
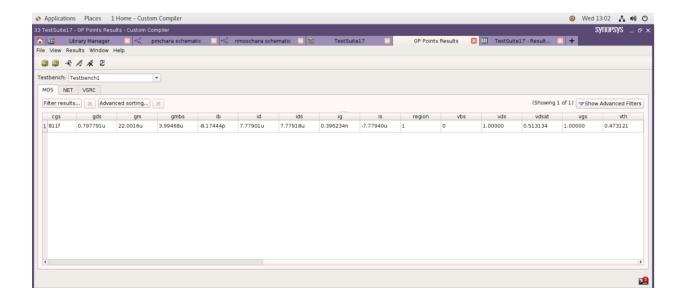
## NMOS gm value to find $\mu_{\text{n}}C_{\text{ox}}$



## **PMOS Schematic**

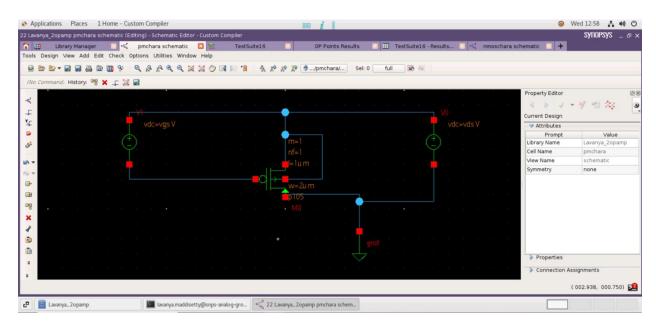

## PMOS gm value to find $\mu_p C_{ox}$

