

Netlist for DC Analysis to check the MOSFETS in Saturation region

```
* Generated for: PrimeSim
* Design library name: Lavanya_2opamp
* Design cell name: opamp1
* Design view name: schematic
.lib 'saed32nm.lib' TT
.param VCM=1.1
*Custom Compiler Version S-2021.09
*Tue Mar 1 10:27:02 2022
```

```
.global gnd!
```

```
*****
```

```
* Library      : Lavanya_2opamp
* Cell         : opamp1
* View         : schematic
* View Search List : hspice hspiceD schematic spice verilog
* View Stop List  : hspice hspiceD
```

```
*****
```

```
xm2 net5 net5 net2 net2 p105 w=7u l=500n nf=2 m=1
xm1 net1 net3 net2 net2 p105 w=87.5u l=500n nf=25 m=1
xm0 net3 net5 net2 net2 p105 w=7u l=500n nf=2 m=1
xm7 vbias vbias gnd! gnd! n105 w=6u l=500n nf=2 m=1
xm6 net4 vbias gnd! gnd! n105 w=6u l=500n nf=2 m=1
xm5 net3 icmr+ net4 gnd! n105 w=3u l=500n nf=1 m=1
xm4 net1 vbias gnd! gnd! n105 w=42u l=500n nf=12 m=1
xm3 net5 icmr+ net4 gnd! n105 w=3u l=500n nf=1 m=1
c9 net3 net1 c=800f
c8 net1 gnd! c=2p
i11 net2 vbias dc=20u
v0 icmr+ gnd! dc='VCM'
v12 net2 gnd! dc=1.8
```

Netlist for AC Analysis to find gain of two stage opamp

* Generated for: PrimeSim
* Design library name: Lavanya_2opamp
* Design cell name: opamp1
* Design view name: schematic
.lib 'saed32nm.lib' TT
.param vicm=1.1
*Custom Compiler Version S-2021.09
*Tue Mar 1 11:05:49 2022

.global gnd!

* Library : Lavanya_2opamp
* Cell : opamp1
* View : schematic
* View Search List : hspice hspiceD schematic spice verilog
* View Stop List : hspice hspiceD

xm2 net5 net5 net2 net2 p105 w=7u l=500n nf=2 m=1
xm1 net1 net3 net2 net2 p105 w=87.5u l=500n nf=25 m=1
xm0 net3 net5 net2 net2 p105 w=7u l=500n nf=2 m=1
xm7 vbias vbias gnd! gnd! n105 w=6u l=500n nf=2 m=1
xm6 net4 vbias gnd! gnd! n105 w=6u l=500n nf=2 m=1
xm5 net3 icmr+ net4 gnd! n105 w=3u l=500n nf=1 m=1
xm4 net1 vbias gnd! gnd! n105 w=42u l=500n nf=12 m=1
xm3 net5 icmr- net4 gnd! n105 w=3u l=500n nf=1 m=1
c9 net3 net1 c=800f
c8 net1 gnd! c=2p
i11 net2 vbias dc=20u
v12 net2 gnd! dc=1.8
v4 icmr+ gnd! dc='vicm' ac=1
v3 icmr- gnd! dc='vicm' ac=-1